

Thursday Sep 12<sup>th</sup>

## CS375 Programming Assignment

In Java, write a program to sum the following sequence.

Use the appropriate Java data type to get 32 bit *floating point*.

$1.0/1.0 + 1.0/2.0 + 1.0/3.0 + 1.0/4.0 + 1.0/5.0 + \dots + 1.0/x$  where  $x = 150,000,000.0$

Compute the sum twice. Once in a loop starting with the first term i.e.,  $1.0/1.0 + 1.0/2.0 + \dots$

The second time, sum the loop from  $1.0/x$  back towards  $1.0/1.0$ .

i.e.,  $1.0/150000000.0 + 1.0/149999999.0 + \dots$

In a separate attached typed document compare and explain your results.

Did you get the same sum when processing the sequence in both directions?

If not, why not?

If your sums are not the same, which of your two sums is the most accurate?

If one is more accurate than the other, why is it more accurate?

Turn in your Java program, the program's output (a screen shot is ok) and the typed explanation.

4, 2, 8, 11, 14, 18, 21, 23

24/28

4.)  $V_{BE} = .7$   $I_B = .1mA$   $30^\circ C$


$V_{BE} = ?$  at  $180^\circ C$   $2mV$  drop / degree increase

~~$180 - 30 = 150^\circ$  increase~~

~~$150 \cdot (2mV) = 300mV$  drop~~

$\therefore V_{BE} \approx .4$  Volts

2.)

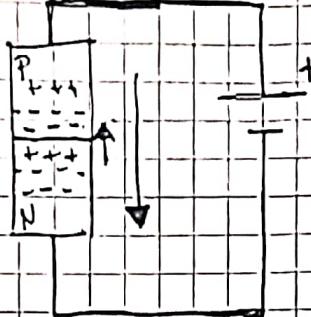


Reverse Biased Emitter-Base Junction  
(~.7V drop from base to emitter)

Forward Biased Collector-Base Junction  
such that current will actually flow  
from collector to emitter

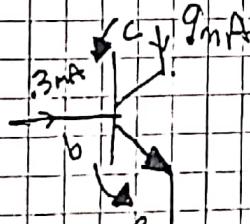8.)

$i_c = 9mA \quad i_b = .3mA \quad i_E = ? \quad \text{Find } \beta \quad \text{be forward b.c. reverse}$



$i_E = \beta i_B = i_c + i_B = 9.3mA$

$i_E = 9.3mA$

$9.3mA = \beta (.3mA)$


$\beta = 30$

~~$\alpha = 30 \quad 30 = 20\alpha \quad 20\alpha = 30$~~

~~$\alpha = 1.5$~~

$\alpha = \frac{\beta}{\beta + 1} = \frac{30}{31} \approx .97$

11.)

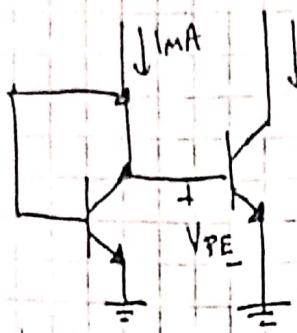

$$I_{E1} = 10 \mu A = 10^{-4} A$$

$\beta = 100$  Find  $V_{BE}$  and  $I_{C2}$

$$I_{mA} = I_{B2} + I_{B1} + I_{C1} \rightarrow I_{mA} = I_{B2} + I_{B1} + 100 I_{B1}$$

$$100 = \frac{i_c}{i_b} \rightarrow i_c = 100 i_{B1}$$

$$I_{mA} = I_{B2} + I_{B1} + 100 I_{B1} \quad I_{B1} = I_{B2}$$

$$I_{mA} = 102 I_{B1} \rightarrow I_{B1} = \frac{I_{mA}}{102} = 9.8 \mu A$$

$$i_{c1} = 100 i_{B1} = 100 (9.8) = 980 \mu A = .98 \text{ mA} = i_{C2}$$

$$\cancel{i_c = \alpha I_{ES} \left[ \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right]} \quad \alpha = \frac{\beta}{\beta + 1} = \frac{100}{100+1} = .99$$

$$i_c = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \quad I_S = \alpha I_{ES}$$

$$9.8 \mu A = \alpha \cdot 10^{-14} \exp\left(\frac{V_{BE}}{26mV}\right)$$


$9.9 \times 10^{-15}$

$$\ln\left(\frac{9.8 \times 10^{-6}}{9.9 \times 10^{-15}}\right) = \frac{V_{BE}}{26mV}$$


seems  
low

$$V_{BE} = .5385 \text{ Volts}$$

16.) B meter design

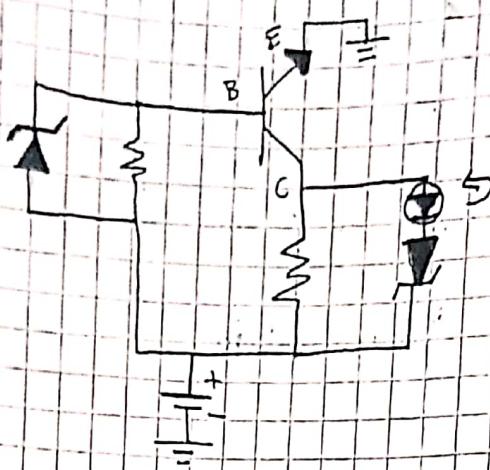

B at least  
meter

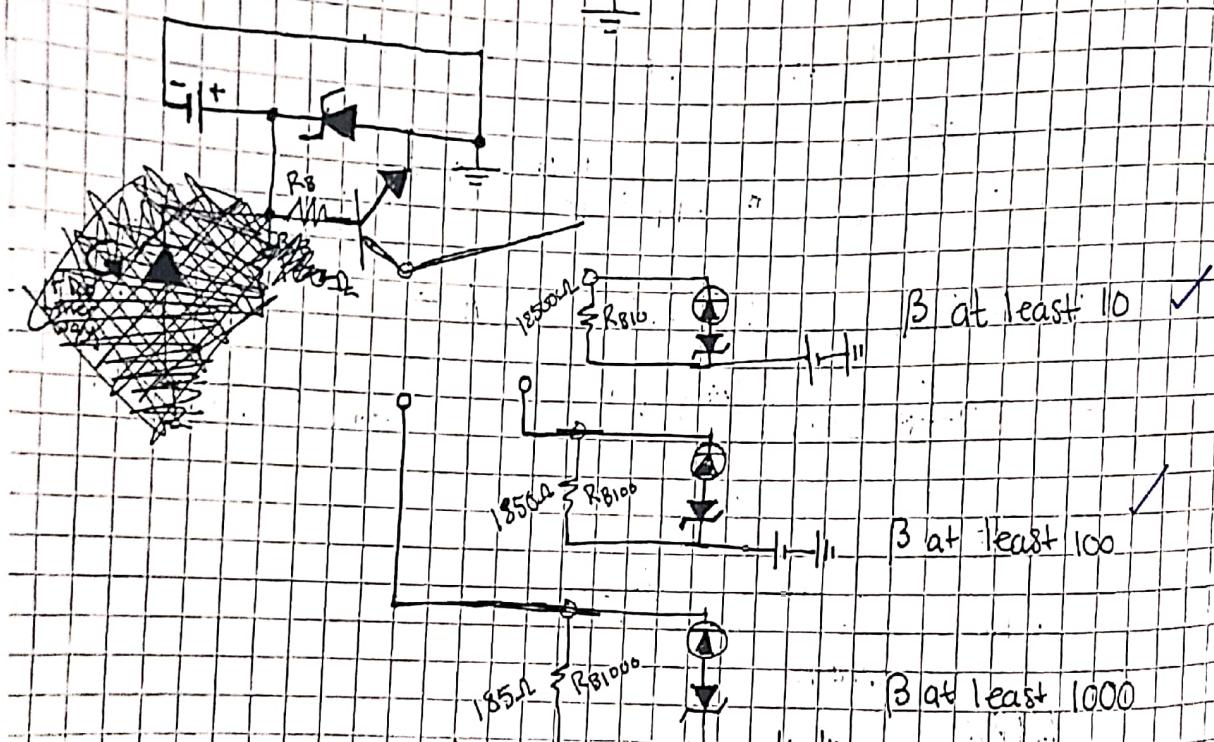

B at least 10 ✓

B at least 100

B at least 1000 ✓

All power  
Sources are  
the same  
battery

So let's find our base current.

Our zener diode makes sure we have 4.7 Volts over  $R_B$ .  
so just use Ohm's Law to find that current.

$$V = IR$$

$$4.7 \div 7 = I_B (100000) \quad / \quad I_B = \cancel{0.054} \text{ mA} = .00004 \text{ Amps}$$

$$\therefore = .04 \text{ mA}$$

(Case  $\beta \geq 10$ )

$$I_C = \beta I_B \rightarrow I_C = 10 (.04 \text{ mA}) = .4 \text{ mA}$$

Assuming our LED has a 2.7 Volt drop, we know  
that  $R_{B10}$  should have  $2.7 + 4.7 \text{ V}$  across it.

Use Ohm's Law again to find  $R_{B10}$  since we know  
the collector current.

$$V = IR \rightarrow 7.4 = I_C R_{B10} \rightarrow R_{B10} = \frac{7.4}{.0004} = 18,500 \Omega$$

(Case  $\beta \geq 100$ )

$$I_C = \beta I_B \rightarrow I_C = 100 (.04 \text{ mA}) = 4 \text{ mA}$$

$$V = IR \quad 7.4 = I_C R_{B100} \quad R_{B100} = \frac{7.4}{.004} = 1850 \Omega$$

(Case  $\beta \geq 1000$ )

$$I_C = \beta I_B \rightarrow I_C = 1000 (.04 \text{ mA}) = 40 \text{ mA}$$

$$V = IR \quad 7.4 = I_C R_{B1000} \quad R_{B1000} = \frac{7.4}{.04} = 185 \Omega$$


So now when the current ~~flows~~ through  $R_B$  is high enough,  
thus meeting the voltage requirements to overcome the diodes,  
the respective LED will turn on indicating the  $\beta$  is at least enough.

This meter doesn't really meet specs and nobody would buy it,  
but it's something.

So are the LED's  
exclusive or summative?  
e.g. how many LED's  
will light up?

$$\beta \approx 100^3$$

21.7

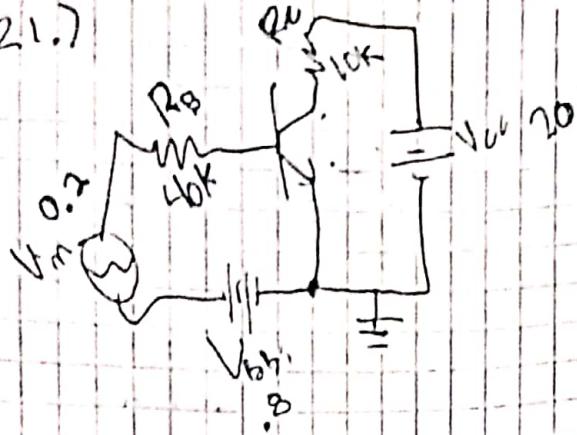

Q point

$$V_{BB} - I_B (40k) = V_{BE}$$


$$8 - I_B (40k) = V_{BE}$$

$$V_{BE} = .8V \text{ at } I_B = 0$$

$$I_B = \frac{.8}{40k} = 20\mu A \text{ at } V_{BE} = 0$$

$$V_{BE} = .8 \pm .2 = 1V, .6V$$
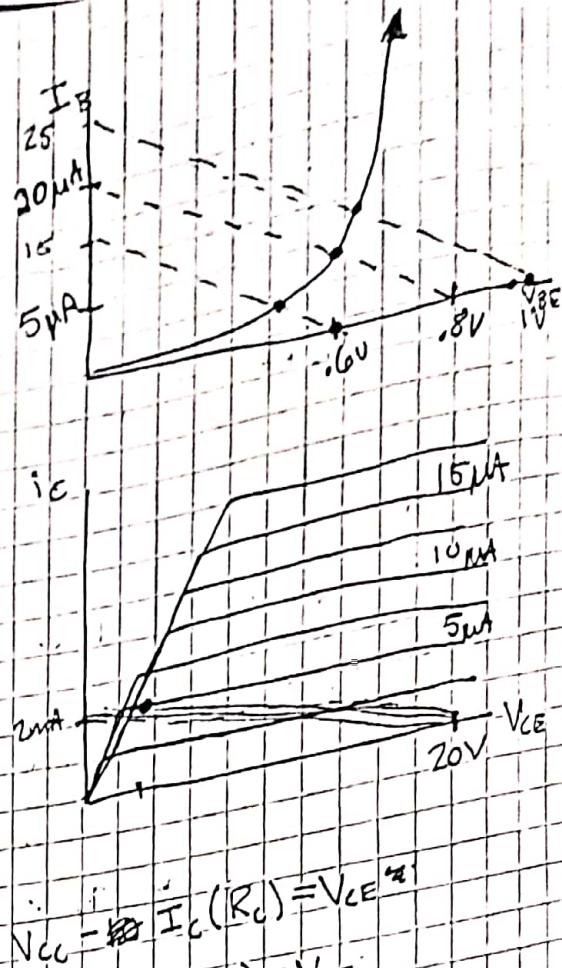
$$I_B = \frac{.8 \pm .2}{40k} = 25\mu A, 15\mu A$$



$$V_{CC} - I_C (R_C) = V_{CE}$$

$$20 - I_C (10000) = V_{CE}$$

$$V_{CE} = 20 \quad I_C = \frac{20}{10000} = .002A = 2mA$$

$$(2\mu A \rightarrow 10\mu A)$$

Since much of this falls in the saturation region, much of this waveform gets clipped at the upper bounds.

Based on the ~~second~~ characteristic graphs above,  $I_C$  looks like anything ~~above~~ the Q point will get clipped.


in what variable?  $V_{BE}$  or  $I_C$ ?

~2 peak-to-peak input  $\rightarrow .4$   $\frac{12V}{.4} = 30 \text{ gain}$   
 ~2.2V to ~2V output  $\rightarrow 12$

I don't know if we should call this an ~~xx~~ gain with 150% upper-clipping or a 150% gain. So to speaker, sketch the waveform and decide then.  $\rightarrow$

Is it a 30 gain or a 150 gain that's half clipped?

23.)

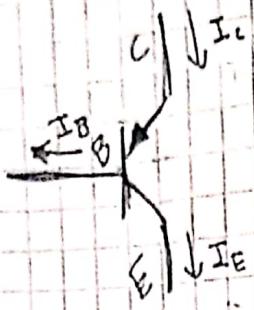

Due Friday 25<sup>th</sup>, Oct

51)  $I = 1\text{mA}$ ,  $V_D = 0.6\text{V}$ ,  $T = 300\text{K}$  Find  $I_s$  at  $n=1$  and  $n=2$

$$I = I_s \left( \exp \left( \frac{V_D}{nV_T} \right) - 1 \right)$$

$$0.001 = I_s \left( \exp \left( \frac{0.6}{0.026} \right) - 1 \right)$$

12/12

$$I_s \approx 9.5021 * 10^{-14} \text{ when } n=1$$

$$0.001 = I_s \left( \exp \left( \frac{0.6}{2(0.026)} \right) - 1 \right)$$

$$I_s \approx 9.743 * 10^{-9} \text{ at } n=2$$

56)  $n=1$ ,  $I=2\text{mA}$ ,  $V_T = 26\text{mV}$

Find equivalent resistance for diode

do the same with 2 in parallel and compare results.

~~$$R = \frac{nV_T}{I_D} = \frac{1(0.026)}{0.002} \approx 13\Omega$$~~

Two in parallel cuts current down to  $1\text{mA}$

$$\text{so } R = \frac{1(0.026)}{0.001} = 26\Omega$$

2  $26\Omega$  resistors in parallel have an equivalent resistance as a  $13\Omega$  resistor. It would seem that this modeling hold true in diode equivalent resistances.

78.)  $n = 1 \quad T = 300K \quad I = 1mA \quad V_D = 600mV$   
 $I = I_s (\exp(\frac{V_D}{nV_T}) - 1)$

How much does voltage need to increase to

- a) double current      b) increase current by 1 order of mag.  
 do these questions again when  $n = 2$

$$I = I_s (\exp(\frac{V_D}{nV_T}) - 1)$$

Let's first find  $I_s$ .  $I_s = \frac{.001}{\exp(\frac{.6}{.026}) - 1} \approx 9.502 * 10^{-14}$

$$.001 = I_s (\exp(\frac{.6}{.026}) - 1)$$

Now let's double current and solve for  $V_D$ . I'm expecting  
 a relationship based on the exponent  $e^y = 2 \quad \ln(2) \approx .6931$

$$.002 = I_s (\exp(\frac{V_D}{.026}) - 1)$$

$$\ln(\frac{.002}{I_s} + 1)(.026) = V_D \approx .618 \text{ Volt} \quad V_D \text{ increased by } \approx 3\%$$

$$.01 = I_s (\exp(\frac{V_D}{.026}) - 1)$$

$$\ln(\frac{.01}{I_s} + 1)(.026) = V_D \approx .65987 \text{ Volt} \quad V_D \text{ increased by } \approx 10\%$$

$$.002 = I_s (\exp(\frac{V_D}{2(.026)}) - 1)$$

$$\ln(\frac{.002}{I_s} + 1)(.026)(2) = V_D \approx 0.6360 \quad V_D \text{ increased by } \approx 6\%$$


$$.01 = I_s (\exp(\frac{V_D}{2(.026)}) - 1)$$

$$\ln(\frac{.01}{I_s} + 1)(.026)(2) = V_D \approx .7197 \quad V_D \text{ increased by } \approx 20\%$$

When  $n$  doubled, so did our proportional increases

Due Wed. Oct 22<sup>nd</sup>

32.)


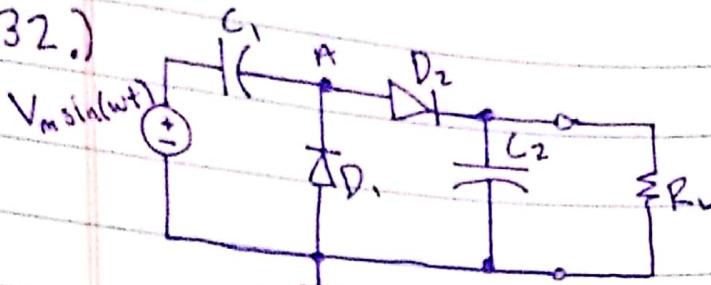


- Sketch voltage of point A against time

- Find Voltage across  $R_L$

- Why called Voltage Doubler?

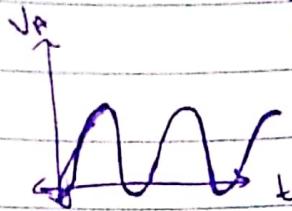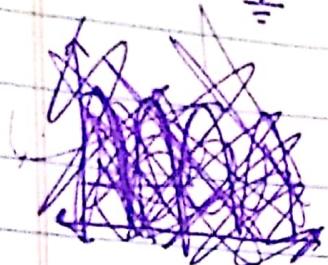
- Find peak inverse voltage across each diode in terms of  $V_m$



$$V_{R_L} \approx 2V_m - (V_{D_1} + V_{D_2}) = V_m + V_{C_1} - V_{D_1} - V_{D_2}$$

↳ if our input peaks at 5 Volts, our output will be roughly 8.8 Volts

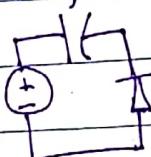When input is in the negative cycle,  $D_2$  is reverse biased and closed as seen here




with  $D_1$  open and forward biased

This acts as a half bridge rectifier charging  $C_1$  to  $V_m - V_{D_1}$ .

Then in the positive cycle  $D_1$  is reverse biased and closed with  $D_2$  forward biased and open. We then see the input voltage +  $V_{C_1} - V_{D_2}$  fall on the  $\approx R_L$  which is our output. This effectively doubles our voltage minus the voltage drop of our diodes.

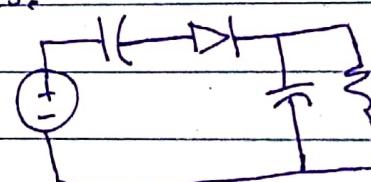I believe  $C_2$  serves to smooth out the rectified signal.




33) Design Clipper Circuit ( $3V$ ,  $-5V$ )

input  $[-10, 10]$  assume  $0.7V$  drop


design for peak current of  $1mA$
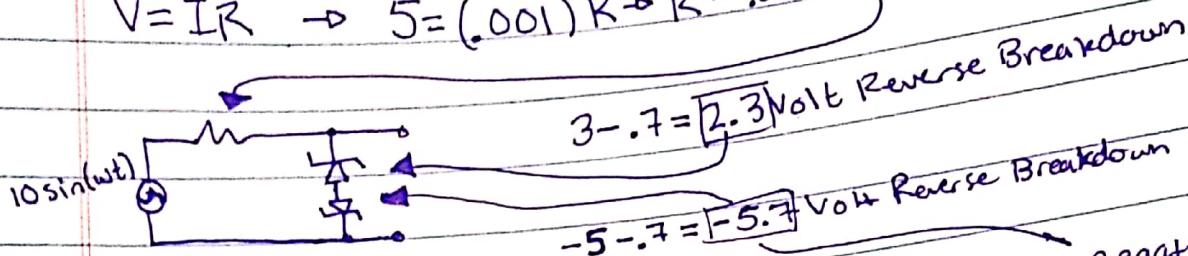
$$V = IR \rightarrow 5 = (0.001)R \rightarrow R = \frac{5}{0.001} = 5000 \Omega$$




This much obvious doesn't work considering the negative breakdown voltage

So let's try something else

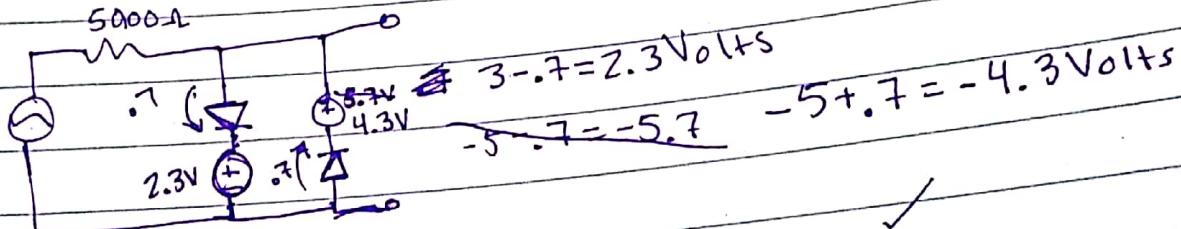

4(e)

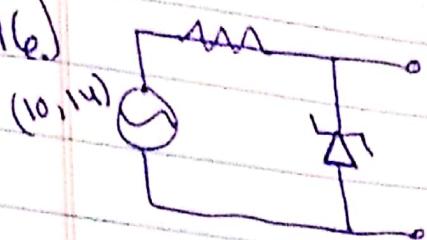

5V Zener voltage  
regulator limit to 5mA

Load Voltage 10-14V  
Load Current 0-10mA

Determine resistance to  
limit diode current

So look at peak case(s)  
(10-14V) and (0-10mA)



This tells us that we do need to limit the current  
on occasion

$$V = IR$$

$$14 = .005(R)$$

$$R = \frac{14}{.005} = 2800$$

since 10V will cause a smaller current across a constant resistor it is not a peak case we care about.

R should be at least 2800Ω to limit the current  
but current will drop when the voltage is not at peak 14 Volts

This is all assuming no all the voltage is lost on the resistor  
which isn't the case. The diode will take either the  
reverse biased 5 Volts or a forward biased 0.7 Volts.  
Let's work in the extreme that puts most voltage  
on the resistor.

$$\text{So } V_R = 14 \text{ Volts} - 0.7 \text{ Volt} = 13.3 \text{ Volt}$$

$$V = IR \rightarrow 13.3 = .005(R) \quad R = \frac{13.3}{.005} = 2660 \Omega$$

So in forward bias we would want  $R = 2660 \Omega$ .

In reverse bias it could be smaller but we need  
to design for the worst case.

This design however severely limits the load  
current. This particular design might have the  
voltage to charge a phone, but at < 5mA Load  
current, I'd hardly even call it a trickle charge.

## electronics HW 5


Ch 3: 3, 5, 7, 8, 10, 15, 19, 20, 24

3.) Zener Diodes

36/36



Adam Stammer

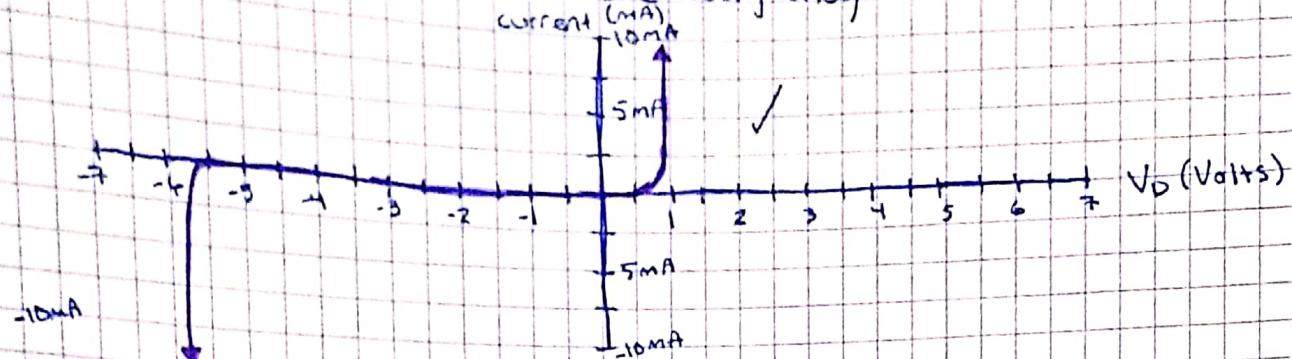breakdown region. Usually they are used when this reverse bias voltage needs to remain constant. Sometimes they are called avalanche diodes or tunneling diodes depending on the breakdown voltage and the effect/phenomena that allows them to work the way they do.





5.)



a)

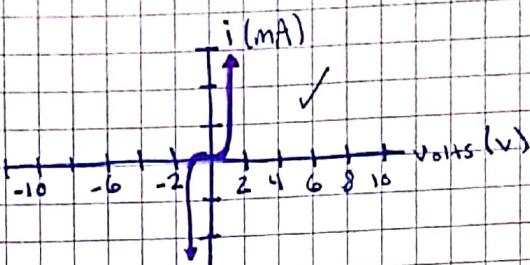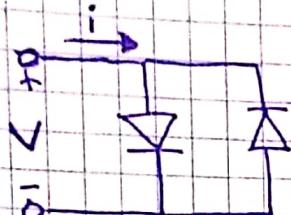

b)

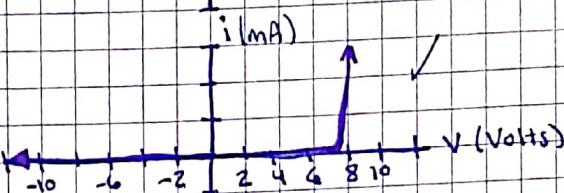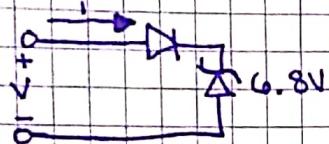

c)

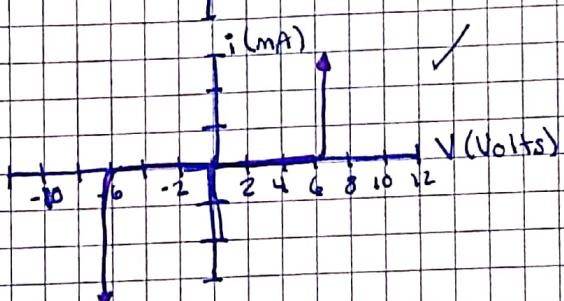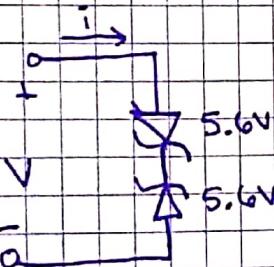

$$7.) \text{ } 25^\circ\text{C} \rightarrow 100\text{mA} \rightarrow 6.5\text{Volts} \rightarrow 650\text{mV} \quad -\frac{2\text{mV}}{1\text{K}} \quad \frac{(650-450)}{x\text{K}}$$

$$\text{ }^\circ\text{C} \rightarrow \text{---} \rightarrow 4.5\text{Volts} \rightarrow 450\text{mV}$$

decrease by  $2\text{mV/K}$ 

Since Celcius and Kelvin have a direct relationship,  $\Delta C = \Delta K$  so yes

$x = 125^\circ\text{C}$  this seems hot to me.  
think about resistors w/ heat sinks!

i) How many reference diodes in series to achieve 3 Volt reference voltage?

3 Volts

$\frac{3 \text{ Volts}}{0.6 \text{ Volts}} = 5$  : 5 diodes of 0.6 forward bias voltage drop could be used in series to achieve 3 Volt reference

What percentage does this change when the temp goes up by 10°C?

$$\frac{-2 \text{ mV}}{1 \text{ K}} \rightarrow \frac{2 \text{ mV}}{10 \text{ K}} \times \text{mV} = -\frac{2}{10} (10) = -20 \text{ mV}$$


So  $\frac{20 \text{ mV}}{0.6 \text{ Volts}} = 33.33\%$

however this change in voltage drop would apply to each diode so the real  $\Delta V_D = -20 \text{ mV} * 5 = -100 \text{ mV}$

$$\text{So } 3 \text{ Volts} - 100 \text{ mV} = 2.9 \text{ Volts output}$$

$$\frac{3 - 2.9}{3} = -\frac{1}{3} \approx -3.33\% \text{ change in the output}$$

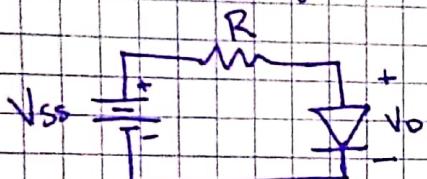10.) Using Figure 3.7 as diode characteristics



Load Line Analysis at  $V_{ss} = 1 \text{ Volt}$  and  $R = 500 \Omega$   
Repeat for  $V_{ss} = 0.5 \text{ Volt}$  and  $R = 500 \Omega$

$$V_{ss} - RI_D - V_D = 0 \quad V_{ss} = 1 \text{ Volt} \quad R = 500 \Omega$$

$$@ I_D = 0, V_{ss} = V_D = 1 \text{ Volt}$$

$$@ V_D = 0, V_{ss} = RI_D \quad I_D = \frac{V_{ss}}{R} = \frac{1 \text{ Volt}}{500} = 2 \text{ mA}$$

$$m_1 = \frac{2 \text{ mA}}{1 \text{ Volt}} = \frac{0.002}{1} = 0.002 = \frac{1}{500} = \frac{1}{R}$$

$$V_{ss} - RI_D - V_D = 0$$

$$@ I_D = 0, V_{ss} = V_D = 0.5 \text{ Volt}$$


$$@ V_D = 0, V_{ss} = RI_D \quad I_D = \frac{V_{ss}}{R} = \frac{0.5}{500} = 0.001 \text{ mA}$$

$$m_2 = \frac{0.001}{0.5} = 0.002 = \frac{1}{500} = \frac{1}{R}$$

$V_{ss}$  does not seem to have an effect on the load line of our diode in this circuit. We can see both quantitatively and qualitatively that the slope for this circuit's load line is  $\frac{1}{R}$ . We've seen this kind of relationship in electronics before, I think. (When we used LEDs)

Solve the I and V of the circuits.  
Assume ideal diodes.

15.) 10V

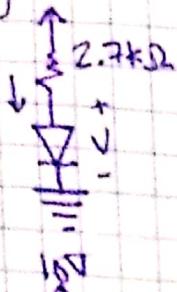

$$V = IR \quad I = \frac{V}{R} = \frac{10 \text{ Volts}}{2.7 \text{ k}\Omega} = \frac{1}{270} \approx 0.037 = 3.7 \text{ mA}$$

No Voltage drop over ideal diode.  $V = 0 \text{ Volts}$

a)


$i \downarrow \leq 2.7 \text{ k}\Omega$

ideal diodes are just open circuits with reverse bias, so no current will flow. This does however put  $V_D = 10 \text{ Volts}$ .

b)




$R_1 \leq 2.7 \text{ k}\Omega$

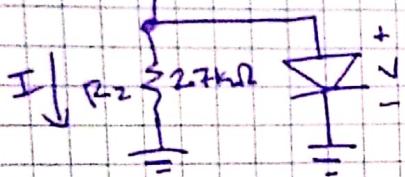


ideal diodes close circuit with forward bias so "all" the current will go through the diode instead of  $R_2$ . That makes this circuit identical to circuit a
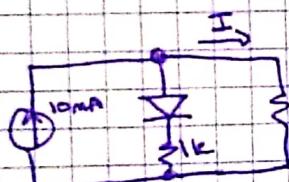
$$I_D \approx 3.7 \text{ mA} \quad I = 0 \text{ mA} \quad V = 0 \text{ Volts}$$



Forward bias so diode closes. Circuit is 2 1kΩ resistors in parallel. Current will split so  $I = 5 \text{ mA}$  and  $V = IR$  so  $V = .005(1000) = 5 \text{ Volts}$

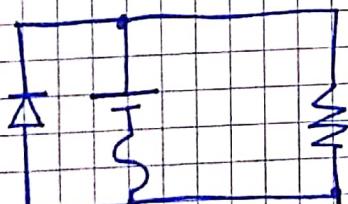19. Build battery protection circuit to avoid reverse polarity causing damage. Use diode(s) and a fuse.







A fuse in series with the battery and a diode in parallel should protect the circuit.


When the battery is placed correctly, the diode is reverse biased and open circuits. The circuit acts as expected, powering the load.

When the battery is placed backwards, the diode is forward biased, conducts electricity, short circuiting the battery and burns out the fuse, which would then need to be replaced.

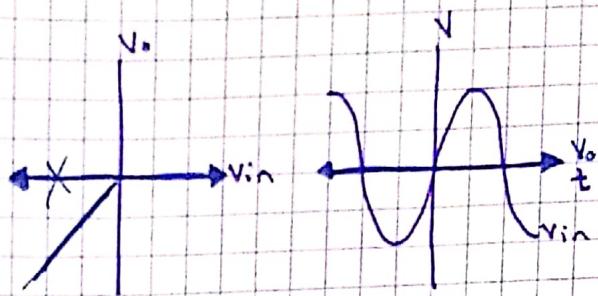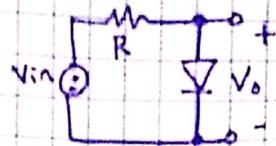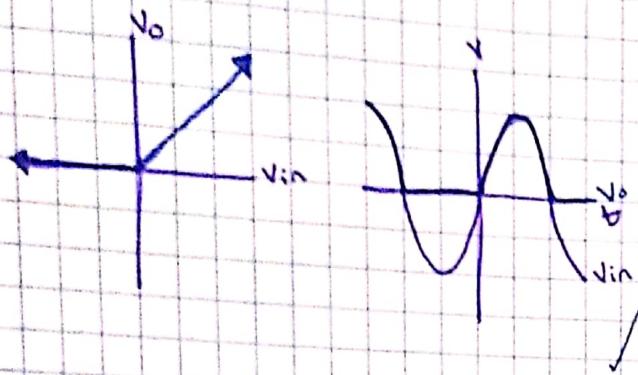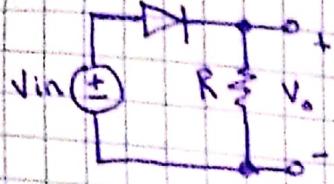o.) Sketch transfer functions for the circuits and plot  $V_o$  against time for  $V_{in}(t) = 10 \sin(200\pi t)$ . Ideal diodes.



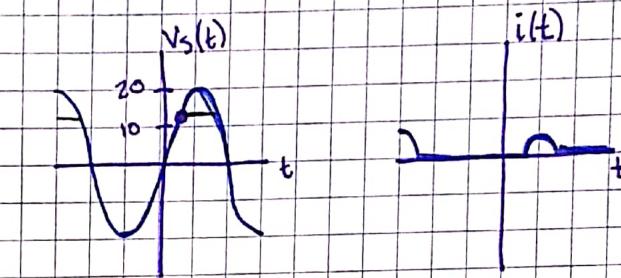24.) Find the peak current, assume ideal diodes.  
Find percentage of cycle the diode is on (conducting).  
Sketch  $V_s(t)$  and  $i(t)$  to scale against time



An ideal diode is on for ~~any~~ any forward bias which would be ~~less than~~ half of the time for a sin wave. So 50%.

The battery will charge and current will flow only when the voltage is above 14V, as seen by the black line.

We can solve for the  $\omega t$  value at the dot marked above. If  $t$  is the first time  $V_{in} \sin(\omega t)$  reaches 14 Volts.  $20 \sin(x) = 14 \rightarrow \sin^{-1}\left(\frac{14}{20}\right) = x$

We also know when it drops below 14 Volts will be mirrored on the other side of the peak. We are also using a period of  $2\pi$  for this calculation. So let's take the time period above 14 Volts and divide it by the total time period to get a percentage of ~~time~~ time when current flows and the battery charges.

$$\frac{\left(\frac{2\pi}{4} + \sin^{-1}\left(\frac{14}{20}\right)\right) - \sin^{-1}\left(\frac{14}{20}\right)}{2\pi}$$

$\approx .25 = 25\%$  of the cycle is used to charge the battery

# Electronics Exam 1


Notes are allowed on the exam. Calculators are also allowed. Computers or internet-able devices are not allowed. Point values for each question are given in parenthesis.

(40)

Adam Stammer

10/10/10 6/1

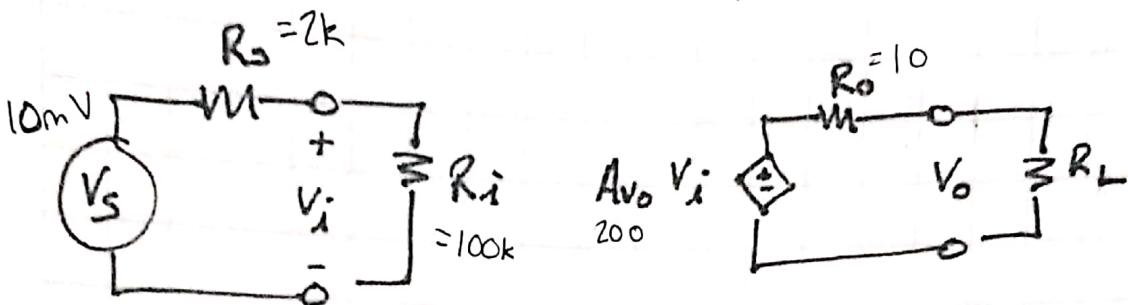1. (10) For the amplifier circuit shown,  $R_s = 2k$ ,  $R_i = 100k$ ,  $A_{v0} = 200$ , and  $R_o = 10$  (all resistance values in Ohms). If  $V_s = 10mV$ , what is the minimum or maximum value of  $R_L$  so that at least  $1.5V$  shows up at the output terminals of the amplifier?



$$V_i = \frac{R_i}{R_s + R_i} (V_s) = \frac{100k}{100k + 2k} \cdot 0.01 \text{ Volts} \approx .0098 \text{ Volts} \approx 9.8mV$$

$$V_L = \left( \frac{R_L}{R_o + R_L} \right) (A_{v0} V_i) = \left( \frac{R_L}{R_o + R_L} \right) (A_{v0} \left( \frac{100k}{100k + 2k} \cdot (.01) \right))$$

$$= \frac{R_L}{10 + R_L} \approx \left( 200 \left( \frac{100}{102} (.01) \right) \right) = 1.5 \text{ Volts}$$

$$= \frac{R_L}{10 + R_L} \left( \frac{200}{102} \right) = 1.5 \text{ Volts}$$

$$\cancel{R_L = 10 \left( 200 \left( \frac{100}{102} (.01) \right) \right) = 20 \Omega + R_L} \quad 10 + R_L = \frac{R_L \left( \frac{200}{102} \right)}{1.5} = R_L \left( \frac{200}{153} \right)$$

$$10 = R_L \left( \frac{47}{153} \right) \Rightarrow R_L \approx 32.55 \Omega$$


~~$$R_L = 10 \left( 200 \left( \frac{100}{102} (.01) \right) \right) = 300 \left( \frac{100}{102} \right) \approx 295 \Omega$$~~

~~so the minimum resistor value would be  
approximately 295Ω to achieve 1.5V on  $R_L$~~

So a  $33\Omega$  resistor will put slightly more than 1.5 Volts on  $R_L$ . A larger resistor will put more of a portion of  $A_{v0}V_i$  on  $R_L$ .

10

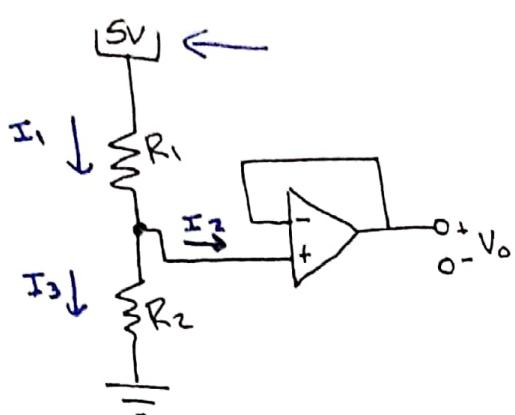2. (10) One problem with a voltage divider (that we found in lab) is that the divider's voltage output is sensitive to the amount of current that's pulled from the output. Specifically, if the load resistance the divider feeds is quite small, the voltage the divider supplies will drop. How can you use an op-amp in conjunction with the divider to create a voltage source that's current-independent? Sketch out a circuit to illustrate your answer.



You could use something  
other than 5 Volts.

Where  $V_+ = \frac{R_2}{R_1 + R_2} (5V)$

Since no current\* will flow into  $V_+$ ,  $I_2 = 0$  which makes

$$I_1 = I_2 + I_3 \Rightarrow I_1 = I_3$$


This would avoid extra voltage drop.

This amplifier could then be used as the input to another amplifier, inverting or otherwise, without current dependence.

\* forgetting bias current ✓

3. (10) You need to amplify a signal by a factor of  $A_{v0} = 30$ . Your incoming source is  $v_s$ . You have only 1k and 10k resistors available. You also have a single LF411 op-amp (schematic shown).
- Sketch out a schematic,
  - also sketch out the wiring diagram connections you'd make to the LF411.
  - You also want to make measurements of the output current from the op-amp. Show how and where the current sensor would be wired.
  - Show where the output voltage would be available.

10

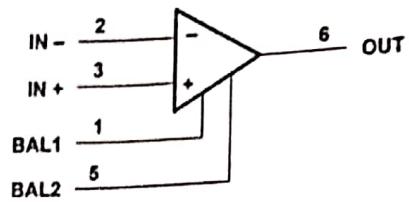

if  $R_1 = 1k$ ,  $R_2 = 29k = 9(1k) + 2(10k)$




So  $R_1$  is 1k

$R_2$  is 9 1k resistors in series with 2 10k resistors



such that  
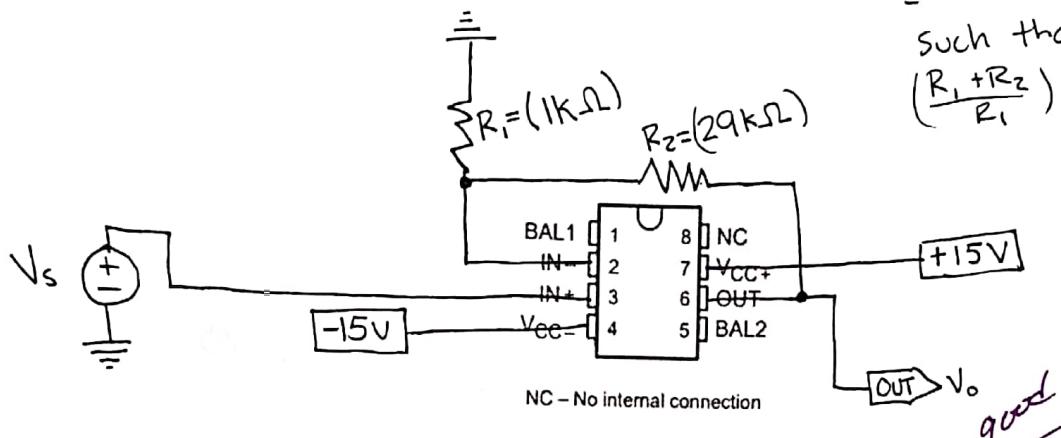
$$\left(\frac{R_1 + R_2}{R_1}\right) = 30$$



$R_1 = 1k\Omega$


$R_2 = 1k\Omega + 10k\Omega = 29k\Omega$

$2 \times 10k$   
in parallel gives 5k

6

4. A graph of open-loop frequency gain vs frequency for a Linear Technologies LT1226 op-amp (\$6.91 each at DigiKey) is shown.

### Voltage Gain and Phase vs Frequency

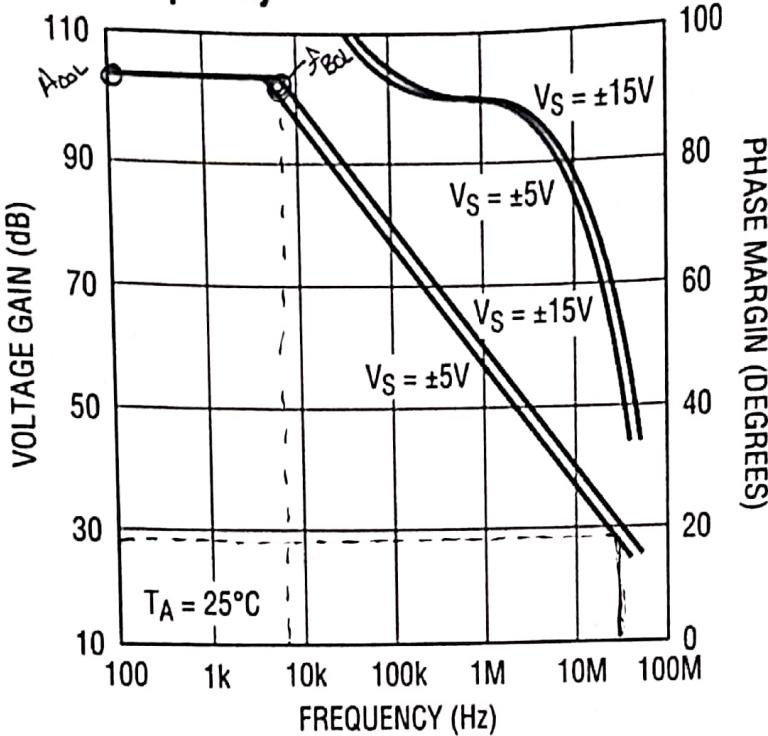

- a. (2) What is the gain-bandwidth product,

$$\begin{aligned} GBP &= f_{BOL} \cdot A_{OOL} \approx 8 \text{ kHz} \cdot 105 \text{ dB} \\ f(t) &= 8000 \text{ Hz} \cdot 10^{\frac{105}{20}} = 1427623528 \end{aligned}$$

1.46 Hz *ok*

- b. (2) the open-loop bandwidth,

$$f_{BOL} \approx 8 \text{ kHz}$$

- c. (2) and what bandwidth do you expect to see from this op-amp if it is designed with a closed-loop gain of  $A_{CL} = 30$ ?

$$20 \log(30) \approx 29.54 \text{ dB}$$


Using the graph above, this corresponds to  $\boxed{40 \text{ MHz}}$

- d. (6) Here is another figure from the same LT1226 spec sheet. If you wanted to amplify a 1mV amplitude sine wave with a closed loop gain of 30, what is the highest frequency you could amplify before the outputted sine wave suffers substantial distortion? Show your work.

$$f = \frac{1}{T}$$

At room temperature our slew rate is roughly 380V/μs at its worst. 1mV amplitude will take us
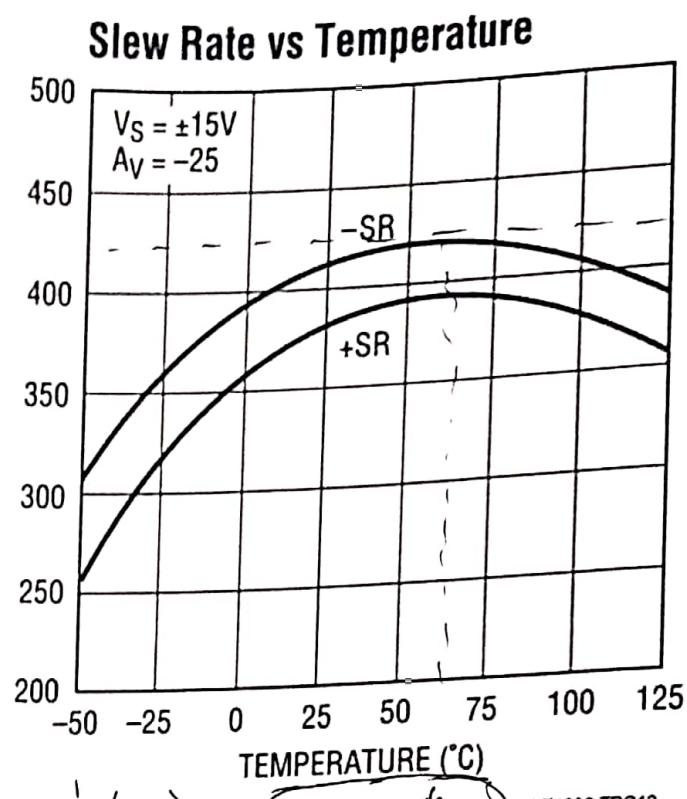
$$\frac{380V}{1\mu s} \Rightarrow \frac{1mV}{x\mu s} = \frac{.001V}{x\mu s}$$



$$x = \frac{1}{380} (.001) \mu s = (2.63 * 10^{-6} \mu s)$$

The rise is half of a slew cycle so I'll multiply this time by two to get the period.  $T = 5.26 * 10^{-6} \mu s = [5.26 * 10^{-12} \text{ seconds}]$

I think you're low by  $\approx 10x$  ~~the derivative is greater~~ I think.

So  $f = \frac{1}{T} \Rightarrow \frac{1}{5.26 * 10^{-12}} \approx [19000 \text{ Hz}]$  So roughly 190 kHz.

Anything faster than this will suffer distortion. Again, this is assuming room temperature and since electronics tend to warm I would consider this to be a high approximation and a dangerous assumption. How much of a problem slew distortion is would depend heavily on the application of the circuit. To be conservative I'd probably use a different op amp for any signal above 150 kHz.